

DI-63 Design Idea

TinySwitch-II

4.8 W CV/CC Charger with Output Cable-Drop Compensation

Application	Device	Power Output	Input Voltage	Output Voltage	Topology
Charger	TNY266PN	4.8 W	85 – 265 VAC	6 V, 800 mA \pm 7%	Flyback

Design Highlights

- Universal input, no-load consumption <300 mW
- Meets CISPR-22 Class B EMI without a Y-capacitor
- Extremely simple circuit, requires only 32 components!
- Circuit has output cable voltage drop compensation
- Ultra-low Leakage current: <5 μ A at 265 VAC input

Operation

Fusible resistor RF1 provides short-circuit fault protection and limits start-up inrush current. Inductors L1 and L2 and capacitors C1 and C2 form a low-cost pi (π) filter that attenuates conducted EMI.

Transformer (T1) has two shield windings (1-3 and 1-open) which reduce the generation of EMI noise. Winding phasing and D7 orientation let no secondary winding current flow when the MOSFET in U1 is ON, so primary winding current stores energy in the core of T1. When the MOSFET in U1 turns OFF, the energy stored in T1 drives current out of the secondary winding, forward biasing D7, charging C7 and developing/maintaining the output

voltage across C7. The V_{BE} of Q1 and the V_Z of VR1 determine the CV set point. The voltage across R4, R5 and the U2-LED determine the CC set point.

Resistors R7, R10 and diode D6 compensate for output-cable voltage-drop. The CV portion of the output VI curve is flat, at the end of the cable, because a current sense resistor (R10) equal to the DC resistance of the output cable is in the voltage feedback loop. Diode D6 implements temperature compensation for the cable drop.

The combination of TinySwitch-II frequency jitter, the output diode snubber (R6 and C5), the T1 shield windings and careful primary clamp circuit component selection enable compliance with CISPR-22, Class B conducted EMI limits, without a Y-1 Safety capacitor. Eliminating the Y capacitor gives this circuit very low (<5 μ A) AC leakage current.

This circuit is suitable for portable electronics chargers.

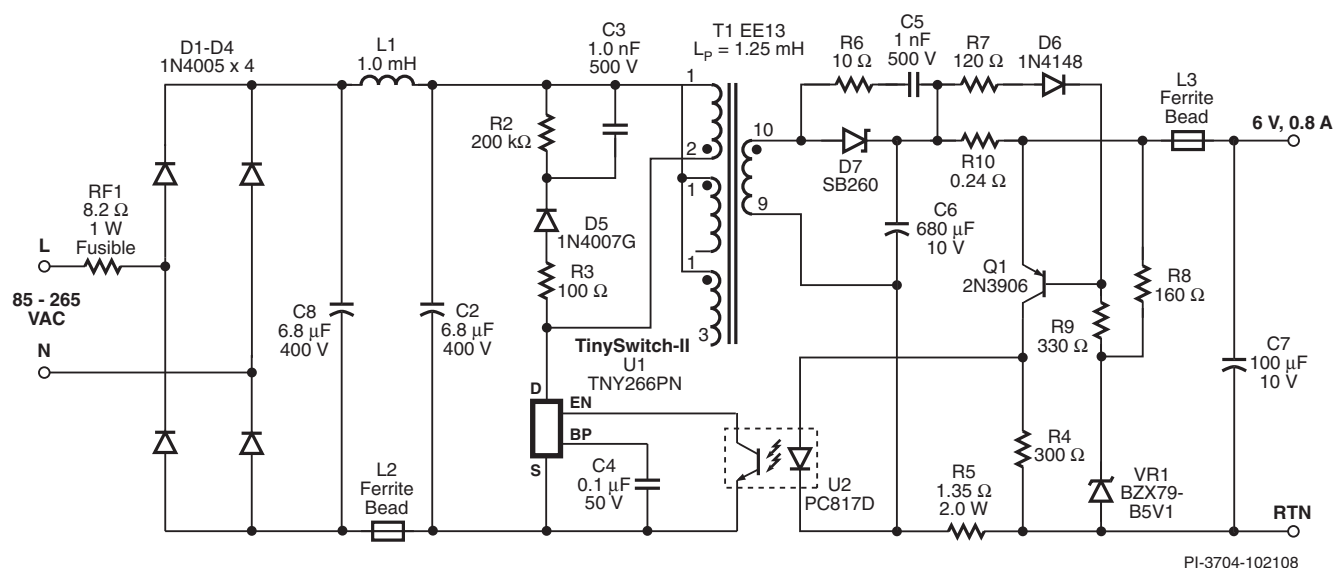


Figure 1. TinySwitch-II Based Charger/Adapter Circuit Diagram.

Key Design Points

- Secondary feedback bias current and output tolerances are minimized by using a low current part for VR1.
- Primary clamp losses are minimized by keeping the voltage reflected across the transformer (V_{OR}) low.
- Picking wire sizes that fill each winding layer produce transformers with the lowest leakage inductance.
- Putting the floating shield winding between the primary and secondary windings reduces EMI noise.
- A high gain opto-coupler (CTR = 200-400) keeps the CC portion of the output curve more vertical.
- R10 should equal the output cable resistance value.

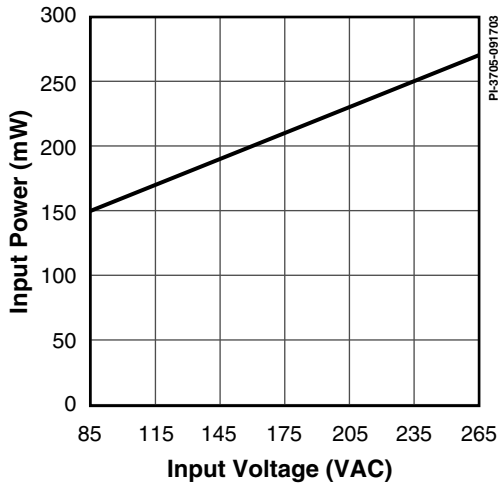


Figure 2. No-Load Input Power vs. Line Voltage.

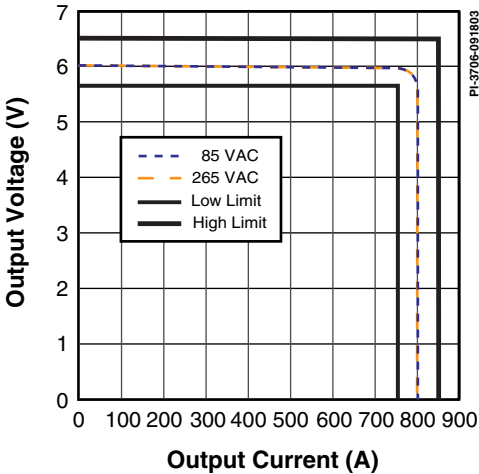


Figure 3. 6.0 VDC, 800 mA CV/CC Curve.

Transformer Parameters	
Core Material	EE16, TDK PC40 or equivalent, gapped for ALG of 127.5 nH/t ²
Bobbin	EE16, 10 pin
Winding Order (pin numbers)	Core Shield (1–3), tape, Primary (1–2), tape, Shield (1–Floating), tape, Secondary (10–9), tape
Primary Inductance	1.25 mH, ±10%
Primary Resonant Frequency	500 kHz (minimum)
Leakage Inductance	35 µH (maximum)

Table 1. Transformer Parameters.

Power Integrations
5245 Hellyer Avenue
San Jose, CA 95138, USA.
Main: +1 408-414-9200
Customer Service
Phone: +1-408-414-9665
Fax: +1-408-414-9765
Email: usasales@powerint.com

On the Web
www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein. POWER INTEGRATIONS MAKES NO WARRANTY HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS. The products and applications illustrated herein (transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com. Power Integrations grants its customers a license under certain patent rights as set forth at <http://www.powerint.com/ip.htm>.

The PI logo, TOPSwitch, TinySwitch, LinkSwitch, DPA-Switch, PeakSwitch, EcoSmart, Clampless, E-Shield, Filterfuse, StackFET, PI Expert and PI FACTS are trademarks of Power Integrations, Inc. Other trademarks are property of their respective companies. ©2003, Power Integrations, Inc.